

National Cheng Kung University  
Department of Electrical Engineering

VLSI Circuits Design

Soon-Jyh Chang Homework#3

**Due Wednesday, May 18, 9am**

TA : Huang-Yu Cheng(黃昱銓) Mail : n26104743@gs.ncku.edu.tw

Problem 1 – Power (30%)

**1A** : Figure 1 shows an 8-input AND gate built by a tree of gates. If all of the input probabilities are 0.5, please **determine** the activity factors and probabilities at each node in the circuit.

※ **X1,X2,X3,X4** are the names of the nodes. (10%)

 


Figure 1. 8-input AND gate

**1B** : Consider an input signal as shown in Fig.2. and its rising and falling time are **100ps**. The clock rate is **1MHz**. **Determine** the activity factor for the signal. (5%)

 


Figure 2. An input signal.

**1C** : Consider a 2-stage inverter buffer drives the capacitor,  $100C_u$ , as shown in Fig.3.

**1C-a**: First, design the circuit with the **minimum delay** and the first inverter input capacitor should be  $4C_u$ . What is the delay you calculate? And what is the size?

**1C-b**: Using Fig.2 as an input signal and using hspice to **measure** the power of circuit you designed in **1C-a**. Additionally, you have to **calculate** the dynamic power and compare with hspice measurement result to **explain** the difference.

※ Assume diffusion capacitors are  $2\text{fF}/\mu\text{m}$  when you calculate the dynamic power.

**1C-c**: Changing the rising and falling time to one-tenth of the clock period and using hspice to measure its power again. Is there any difference between **1C-b** and **1C-c**? If so, please briefly explain it. (15%)

**Note:**

1.  $C_u = 1\text{fF}$ .
2. Assume  $CG = 2\text{fF}/\mu\text{m}$ .
3.  $Kn'/Kp' = 3/1$
4. All transistors use minimum length.

 


Figure 3. 2-stage inverter diagram.

```

*** clock_rate 1MHz
.param clock_rate = 1Meg
.param clk_period = 1/clock_rate
.param td = 100p
*** vin
vvin vin gnd pwl(
+ 0 0v
+ 'clk_period-td/2' 0v
+ 'clk_period+td/2' 1.8v
+ .....
*** omission ***
+ .....
***
.tran 1p '10*clk_period'
*** meas power
.MEAS      power_avg  AVG  power

```

Figure 4. Reference code.

## Problem 2 – Ring Oscillator(40%)

In many applications, we need to generate the clock signal in the chips. Therefore, the ring oscillator would be adopted. Fig.5. shows an N-stage ring oscillator using conventional inverter.

 


Figure 5. Ring Oscillator Circuit


**2A** Please derive and design a ring oscillator with **frequency of 3GHz**, and **the duty of the ring oscillator should be  $50\% \pm 1\%$** . Finally, simulate it with HSpice.

**Note: An initial condition at some node in the circuit is required**

**2B** Create the layout of the ring oscillator you design in **2A** and run the post-layout simulation(R+C+CC). Make sure the **frequency is 3GHZ and the duty is  $50\% \pm 1\%$**  and paste the result in the report. Please show the “No Error Figure” of the DRC and LVS verification, and paste the layout figure.

**2C** Fig.3 illustrate a Voltage-Controlled ring Oscillator (VCO). The control signals,  $V_{ctrl}$  and  $\overline{V_{ctrl}}$ , are used to control the current source so that the delay can be controlled by the signals. Please derive and design a VCO that the center frequency is **3GHz** when  $V_{ctrl} = \overline{V_{ctrl}} = 0.9V$ . Furthermore, the frequency should **cover from 2.9G to 3.1GHz** when  $V_{ctrl} = 0.7\sim 1.1V$  and  $\overline{V_{ctrl}} = 1.8V - V_{ctrl}$ . Finally, simulate it with HSpice.

**Note: An initial condition at some node in the circuit is required**

 

**Figure 6. Voltage-Controlled ring Oscillator**

```
.meas tran period trig v(vin) val=0.9 fall=10 targ v(vin) val=0.9 fall=11
.meas tran frequency param='1/period'
.meas tran t_on trig v(vin) val=0.9 rise=10 targ v(vin) val=0.9 fall=11
.meas tran duty_cycle param='t_on/period'
```

**Figure 7. Reference mearsurement code**

### Problem 3 - Power Delay Product(30%)

A 2-input static CMOS NAND gate with N-stage **inverting** buffer to drive the capacitor,  $500C_u$ , as shown in Fig.8.

**3A** : Consider the circuit in Fig.8. How many stages will give the **minimum delay**, and how should the stages be sized? Furthermore, assume we **neglect the diffusion capacitances**. If the delay constraint is **between  $30\tau$  and  $29\tau$** , what N should be set to give the **lowest power**, and how should the stages be sized? How much dynamic power does it consume?

※Clearly present your procedure with explanation and states your assumptions, if any.

#### Note:

1. Each input capacitor of NAND is  $10C_u$
2.  $C_u = 1\text{fF}$ .
3. Assume  $CG = 2\text{fF}/\mu\text{m}$ .
4.  $Kn'/Kp' = 2/1$
5. All transistors use minimum length.

 


Figure 8. 2-input NAND with N-stage **inverting** buffer

**3B** : Consider the circuit shown in Fig.9. How should the stages be sized to get the **minimum Power Delay Product**?

#### Note:

1.  $C_u = 1\text{fF}$ .
2. Assume  $CG = 2\text{fF}/\mu\text{m}$ .
3.  $Kn'/Kp' = 2/1$
4. All transistors use minimum length.
5. Each input capacitor of NAND is  $10C_u$

 


Figure 9. 2-input NAND with 1-stage **inverting** buffer

**3C** : Consider the circuit in **3B** with the two input signals, A and B, illustrated in Fig.10. However, the input order of 2-input static NAND gate can affect the delay. Please derive the propagation rising delay ( $t_{pdr}$ ) and the propagation falling delay ( $t_{pdf}$ ) of NAND first to get the correct input order. **Clearly present your procedure with explanation and state your assumptions, if any.**

※Hint: You should consider the worst case with the input order.

Then, please sweep the sizes of the inverter to get the **figure of Power Delay Product**, and explain it on the report. According to the figure of Power Delay Product, choose the **best one sizes** and fill the Table.1.

Inverter size	$t_{pdr}$	$t_{pdf}$	$t_{pd}$	$P_{avg}$	$t_{pd} \cdot P_{avg}$
(Pmos_size)					
(Nmos_size)					

Table.1 the best sizeds chosen from the minimum PDP.

 


Figure 10. Input signals

```

.meas tran rising_delay
+trig v(vin)    val=0.9 td=td rise=5
+targ v(vout)   val=0.9 td=td rise=5
.meas tran falling_delay
+trig v(vin)    val=0.9 td=td fall=5
+targ v(vout)   val=0.9 td=td fall=5
.meas tran delay_avg
+param = '(rising_delay+falling_delay)/2'
.meas tran power
+avg p(vdd) from=td to=run_time
.meas tran pdp
+param='abs(delay_avg*power)'

```

Figure 11. Reference measurement code.

-----Important Notes-----

1. 12pt character size in your report.
2. Please invert the color of all your schematics, waveforms and layout.
- 3. DO NOT COPY**
- 4. No late homework will be accepted. When it is due, it is due.**
5. It is needless to print your report. Please compress the needed files and report shown as below. Then upload your compressed file to moodle website.

