

**National Cheng Kung University**  
**Department of Electrical Engineering**

**VLSI Circuits Design 2022**

Soon-Jyh Chang    **Homework#5**

TA : Kuang-Yu Teng(鄧光宇)    [dominant@ssc.as.ee.ncku.edu.tw](mailto:dominant@ssc.as.ee.ncku.edu.tw)

Due on 2022/06/15 ,Wednesday ,9:00

Use 'cic018.l', TT corner, VDD = 1.8V to do every simulation.

**Problem 1 - Design 6T SRAM**

**1A**

Please design a 6T-SRAM(as shown in Fig.1) with the clock signal(CLK) and control signals (WE and RE). WE is write enable mode, and RE is read enable mode. You should use pre-charge circuit, read circuit and write circuit to enable 1-bit READ and WRITE function work correctly.

(**Hint** : You can refer to pages 16 of Unit 46 : Memories in lecture notes )

You should simulate the following four patterns to check your design can work correctly:

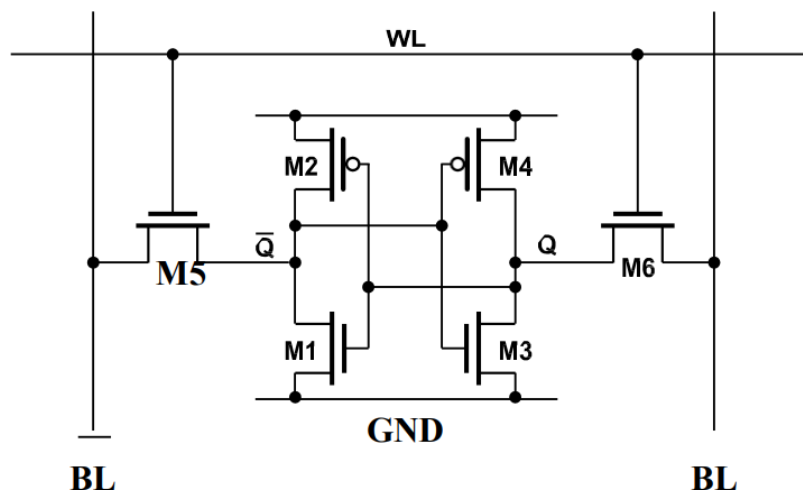


Fig.1 6T SRAM cell


- (1) The stored data(Q) is 0, RE is **HIGH**.
- (2) The stored data(Q) is 1, RE is **HIGH**.
- (3) The stored data(Q) is 0, WE is **HIGH**, write data is 1.
- (4) The stored data(Q) is 1, WE is **HIGH**, write data is 0.

Please paste the simulation result in your report with the following signals: CLK, WE,

RE, WL,  $V_{\text{write\_data}}$ , BL, BLB, Q, and QB.

For example, if we want to write 1, the WE will turn on and RE will turn off.

Then, Q will change from 0 to 1.

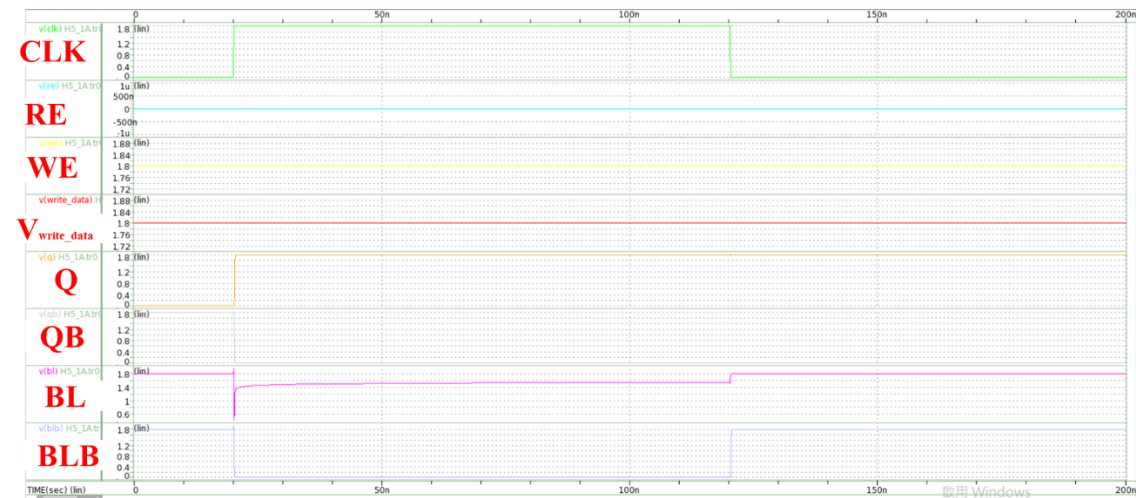

## 1B

Please estimate the read static noise margin (SNM) of the SRAM cell you design in

**1A**. The method is described as follows:

First, the feedback from the cross-coupled inverters is broken and note that the wordline and bitline are held at VDD during a read, as shown in Fig.2(a).

Next, the VTC(Voltage Transfer Curve) of the “inverter” formed by half of the SRAM cell is found by sweeping  $V_1$  (the inverter’s input) from 0 to VDD and measuring  $V_2$  (the inverter’s output). This plot is then used to construct the “butterfly plot”, which is representative of the two halves of the cell driving each other, as shown in Fig.2(b).

The read SNM is the side length of the maximum possible square that can fit inside of the butterfly plot.

You do not have to calculate the size of this maximum square, but you should submit the butterfly plot (generated by HSPICE or other software) and graphically indicate the SNM. (**Note**: only simulate the 6T-SRAM without any other control signals.)

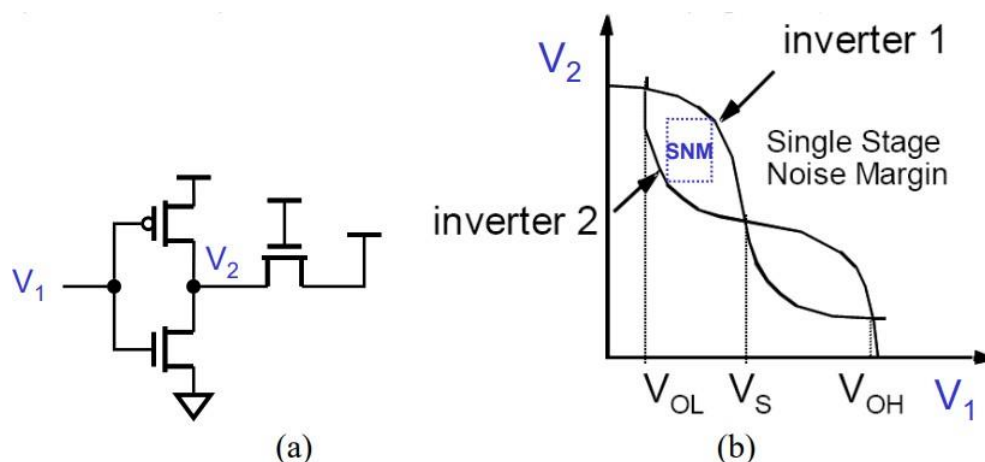


Fig.2 (a)Testing method of the read SNM (b)The butterfly plot used to find SNM

## 1C

Please estimate the write noise margin (WNM) of the SRAM cell you design in **1A**. The method is described as follows:

During a write, VDD is applied to the wordlines, and the value to be written into the memory cell is driven onto the bitlines. Again, the feedback from the cross-coupled inverters is broken, and the VTC of the “inverters” are measured. Note however that in this case, the VTCs of the two halves of the SRAM are no longer the same (since one of the bitlines is driven to 0V, while the other to VDD), as shown in Fig.3(a). These VTCs are used to create a butterfly plot, and the WNM is the side length of the largest square that can fit inside of the butterfly plot, as shown in Fig.3(b).

You do not have to calculate the WNM, but you should generate the butterfly plot (again by HSPICE or other software) and graphically indicate the WNM. (**Note:** only simulate the 6T SRAM without any other control signals.)

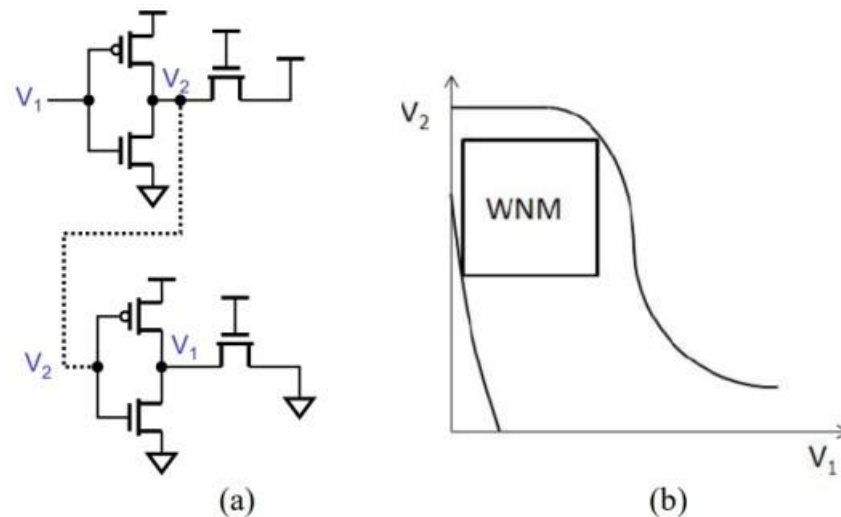


Fig.3 (a)Testing method of the WNM (b)The butterfly plot used to find WNM

## Problem 2 – Characterizing Sequencing Element Delay

### 2A

Fig.4 shows a latch. Assume that the latch is loaded with fan-out of 3.

The size of transmission gate:  $(\frac{W}{L})_p = \frac{1.5\mu m}{0.18\mu m}$  ,  $(\frac{W}{L})_n = \frac{1.5\mu m}{0.18\mu m}$

The size of inverter:  $(\frac{W}{L})_p = \frac{1\mu m}{0.18\mu m}$  ,  $(\frac{W}{L})_n = \frac{0.5\mu m}{0.18\mu m}$

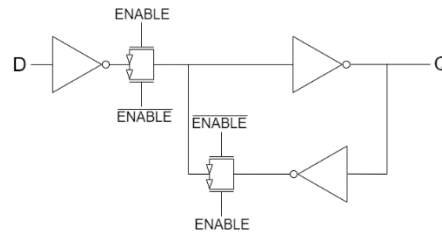


Fig.4 latch

Please use HSPICE to find  $t_{setup}$ ,  $t_{ccq}$  and  $t_{pdq}$  of a latch and finish the following sheet.

( $t_{pdq}$  is 5% greater than minimum value of  $t_{dq}$ )

You should use **ENABLE**,  **$\overline{ENABLE}$**  and  $V_{data}$  with the falling and rising time of 80ps as shown in Fig.5 to simulate.

	$t_{setup}$	$t_{ccq}$	$t_{pdq}$
value			

(Hint: you may use PWL(  $t_1$   $v_1$   $t_2$   $v_2$   $t_3$   $v_3$ .....) or Pulse ( $v_1$   $v_2$   $t_d$   $t_r$   $t_f$  width period))

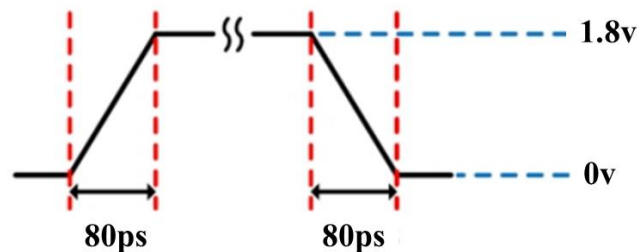


Fig.5 The falling and rising time of **ENABLE**,  **$\overline{ENABLE}$**  and  $V_{data}$

You can refer to the following code to calculate the  $t_{dcr}$ ,  $t_{cq}$  and  $t_{dq}$ .

```
.measure tran tdc trigg v(D) val=0.9 rise=1 targ v(clk) val=0.9 rise=1
```


### 2B

Please use waveview to plot the curve of  $t_{dcr}$  VS  $t_{cq}$  and  $t_{dcr}$  VS  $t_{dq}$  and merge into one figure.
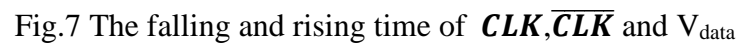
### 2C

The size of transmission gate:  $(\frac{W}{L})_p = \frac{1.5\mu m}{0.18\mu m}$  ,  $(\frac{W}{L})_n = \frac{1.5\mu m}{0.18\mu m}$   
The size of inverter:  $(\frac{W}{L})_p = \frac{1\mu m}{0.18\mu m}$  ,  $(\frac{W}{L})_n = \frac{0.5\mu m}{0.18\mu m}$

You should use ***CLK,  $\overline{CLK}$***  and  $V_{data}$  with the falling and rising time of 80ps to simulate as shown in Fig.7.



	$t_{\text{setup0}}$	$t_{\text{pcq0}}$	$t_{\text{ccq0}}$	- $t_{\text{hold0}}$
value				
	$t_{\text{setup1}}$	$t_{\text{pcq1}}$	$t_{\text{ccq1}}$	- $t_{\text{hold1}}$
value				
	$t_{\text{ar}}$	$t_{\text{af}}$		
value				

	explain
$t_{\text{setup0}}$	
$t_{\text{pcq0}}$	
$t_{\text{ccq0}}$	
$- t_{\text{hold0}}$	
$t_{\text{setup1}}$	
$t_{\text{pcq1}}$	
$t_{\text{ccq1}}$	

$-t_{hold1}$	
$t_{ar}$	
$t_{af}$	

## 2D

Please use waveview to plot the curve of  $t_{dc}$  vs  $t_{cq}$  concluding four cases(**D rises Q rises**, **D rises Q falls**, **D falls Q rises**, **D falls Q falls**) and merge into one figure.

(**Note** : You should sweep the same time when you merge four cases  $t_{cq}$  into one figure.)

### Note:

1. It is needless to print your report. Please compress the needed files and report shown as below. Then upload your compressed file to moodle website.12pt character size.
2. 12pt character size in your report.
3. Change the background color of all your figures, schematic, and waveforms, to white.
4. **Do not copy**
5. **No late homework will be accepted. When it is due, it is due.**

